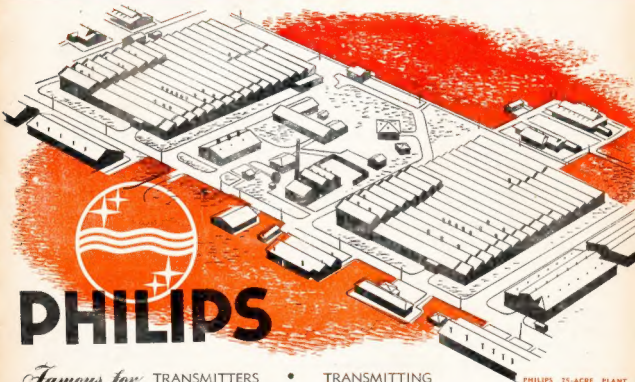


AMATEUR RADIO

MARCH
1948

JOURNAL OF THE WIRELESS INSTITUTE OF AUSTRALIA



PHILIPS

Famous for TRANSMITTERS • TRANSMITTING
COMPONENTS • TRANSMITTING TRIODES, TETRODES
AND PENTODES • HIGH VACUUM AND MERCURY
VAPOUR RECTIFIERS.

PHILIPS 75-ACRE PLANT
AT HENDON, SOUTH AUS-
TRALIA. THREE PHILIPS
FACORIES ARE COM-
BINED IN THIS MODERN
PLANT.

PHILIPS ELECTRICAL INDUSTRIES OF AUSTRALIA PTY. LTD.

SYDNEY • MELBOURNE • ADELAIDE • PERTH • BRISBANE



FOR THE EXPERIMENTER & RADIO ENTHUSIAST

Registered at G.P.O., Melbourne, for transmission by post as a periodical.

6^{d.}



1948



Don't

SIT BACK & CURSE!

Get AM/FM (NB*) AT WILL!

Kingsley's research engineers are perfecting an AM/FM (*narrow band) adaptor for use with "Ham" communication receivers and it is expected that it will be released shortly—probably next month.

Don't sit back and curse when one of the fellows calls you on F.M. — flip the switch and be in a position to give him a critical report.

Watch for further announcements!

K/S9'er—Many hams are delighted with the performance of the Kingsley.

K/S9'er Signal Booster—6, 10, and 20 metre bands; also with the Kingsley Short Wave Converter type KF/C6 for use on the 6 metre bands.

Send for full particulars of each.

IMPORTANT!

If your usual supplier is unable to supply your requirements of Kingsley Products, drop us a line mentioning his name and address.

Ask for—Insist on—DEMAND—genuine Kingsley Parts from your supplier!



KINGSLEY RADIO

KINGSLEY RADIO PTY. LTD.

380 St. Kilda Road, Melbourne, Victoria . Phones: MX 1159, MX 3653

EDITOR:

T. D. HOGAN, VK3HX,
Telephone: UM 1732.

MANAGING EDITOR:

J. G. MARSLAND, VK3NY.

TECHNICAL EDITOR:

J. C. DUNCAN, VK3VZ.

COMPILATION:

R. W. HIGGINBOTHAM, VK3RN.

DISTRIBUTION:

H. N. STEVENS, VK3JO.

ADVERTISING REPRESENTATIVE:

W. J. LEWIS,
20 Queen Street, Melbourne, C.I.
Telephone: MU 5154.

Printers:

H. HEARNE & CO. PTY. LTD.,
285 Latrobe Street, Melbourne.

MSS. and Magazine Correspondence should be forwarded to the Editor, "Amateur Radio," Box 2611W, G.P.O., Melbourne, on or before the 15th of each month.

Subscription rate is 6/- per annum, in advance (post, paid).

Wireless Institute of Australia (Victorian Division) Rooms. Telephone FJ 6997.

— IN THIS ISSUE —

Band Switching Converter for V.H.F.s.	3
Flexlax Conversion Exciter Unit	6
Grid Drive	8
Calculating Distance of QSOs	8
Writing an Article	9
Such Nice People	11
Station Description	12
Plate Modulating the Beam Tetrode	12
Fifty and Up	14
Federal, QSL, and Divisional Notes	15
Correspondence	24

AMATEUR RADIO

*Published by The Wireless Institute of Australia,
Law Court Chambers, 191 Queen Street,
Melbourne, C.I.*

EDITORIAL



BAND OCCUPANCY

Probably the most important question confronting the Radio Amateur to-day is the international allocation of frequencies, and in particular, how he will fare in the matter of allocation of Amateur Bands.

The Wireless Institute of Australia has been fortunate in having enjoyed close and sympathetic co-operation with the Postmaster-General's Department whose Radio Inspectors have done their utmost to facilitate the use by Amateur Stations of as much of the Spectrum as possible under the existing international plan.

Under the new allocations determined at Atlantic City, Amateurs will receive several new bands which will serve in some measure to offset the loss of other portions of the spectrum which we have had to accept with considerable reluctance.

The vital thing for Amateurs to remember is that these new bands must be used adequately and as quickly as possible unless we are prepared to suffer criticism for their disuse.

The Federal Executive is now discussing with the Department the question of Amateur Bands in our zone, and it is essential that we shall be able to give an assurance that when the com-

plete allocations are promulgated immediate use will be made of them.

One of the most difficult problems confronting the Federal Executive is to explain why the twenty metre band is so sadly misused for short haul contracts which could be carried out on V.H.F. bands and also why such lengthy conversations on trivial matters continue to cause congestion on a band which we are always claiming is too narrow now to accommodate all our stations.

In view of the increase in Amateur Stations throughout the world, we need to employ our bands to the best advantage or we can be sure that the ever-watchful commercial interests will endeavour to whittle down our hard won bands until there is nothing left except on extremely high frequencies.

The same argument can be used for the use of frequency modulation and pulse transmissions, the retention of which we may one day be asked to justify.

The Federal Executive intends to organise suitable contests to popularise the newer bands, but the influx to these new regions lies with each and every Amateur who is a true experimenter and really wants to enjoy Amateur Radio to the full.

W.R.G.

Homecrafts

PTY. LTD.

MAGNETIC VALUES YOU CAN'T RESIST!



RADIOGRAM CABINETS

Walnut Piano Finish
Reduced from 19 gns. to
15 gns.



CARBON RESISTORS

Reduced from 6d. each to
6d. dozen.

ELECTRIC GRAMOPHONE PICKUPS

Reduced from 70/- to
25/11

HOMEBROADCASTER MICROPHONES

Reduced from 17/6 to
7/11

POWER TRANSFORMERS

80 ma. Reduced from 22/6
to 15/11

TELEPHONES

with 10 mile range. Com-
plete. Reduced from 10 gns.
to 2 gns.

2 GANG CONDENSERS

Reduced from 18/6 to 6/11

LARGE FULL VISION DIALS

Reduced from 25/- to
12/11

CRYSTAL PICKUP CARTRIDGES

Build your own Crystal Pick-
up. Reduced from 30/- to
18/11.

Small 12v. GENERATORS,
originally £3,
Cut to 15/11



5 BP 1 5in.

CATHODE RAY TUBES

Cost £15. Now

37/6

(plus Tax)

Also Circuit Blue Print of Cathode
Oscillograph, 1/6

6" LOUD SPEAKERS
Per mag Type. Reduced
from 39/6 to 23/11

ELECTRIC SOLDERING IRONS

100 watt. Reduced from
29/6 to 12/11

200 mfd 12 Volt CON-
DENSERS. Reduced from
4/- to 1/3

12 Volt GAS FILLED
VIBRATORS. Reduced
from 30/- to 9/11

Large 12 Volt GENERA-
TORS. Will charge 12 volts
up to 100 amps. Suitable
for Home Lighting Plants.
Cost £60. Reduced to
15 gns.

Put this out for future reference

290 Lonsdale St. C. 4311

MELBOURNE:

Also at

211 Swanston Street.

SYDNEY:

100 Clarence Street.

BALLARAT:

307 Sturt Street.

NEWCASTLE:

26 Hunter Street.

GEELONG:

132a Moorabool Street.

TASMANIA:

Hobart, Launceston and
Burnie.

A BAND SWITCHING CONVERTER FOR THE V.H.F.s.

BY J. C. DUNCAN*, VK3VZ

In common with many other Amateurs who are now contemplating ways and means of venturing into the High Frequency spectrum, the writer felt the need of increasing the operating range of the normal station receiver, so that reception would be available up to the 166 Mc. band. In addition the performance of all receivers used on the lower frequencies, shows a marked falling off in performance above 22 Mc. so that any converter, which is the logical way of making this expansion, should start at the 28 Mc. band, followed by the 50-54 Mc. and then the 166-170 Mc. band.

Another important point to be considered is the fact that quite a few Amateurs are in possession of receivers from Disposals, which only go as high as 22 Mc., which also indicates 22 Mc. as the starting point.

In the writer's case the station receiver is an AMR200, which is the Australian version of the Super Pro, and it was decided that the converter be mounted in the compartment in the power supply chassis, which normally houses the power lead and cables. This compartment is quite small, being 7" high, 3 1/2" wide, and 12" deep, hence the unusual shape of the Converter, for due to the lack of available space, it was necessary to utilize every square inch available. Another problem which had to be solved here was the one of band changing, and it was obvious that the only way would be band switching. Frankly the writer was very dubious of switching coils at 166 Mc., but was amazed to find that results on this band compared more than favourably with an A.S.V. receiver, and showed a marked superiority in signal to noise ratio.


Before commencing with the design and construction of the Converter, it was decided to use an old converter which the writer had on hand, to conduct some experiments to determine whether it would be possible to use some form of dial-less converter, or broad band r.f. stages, and thereby simplify the design. Results in this direction were disappointing, and the conclusion was reached that these methods are satisfactory if one is willing to accept reduced performance. The first test was made along the dial-less converter lines, the converter oscillator was fixed at 20 Mc. and the receiver tuned between the limits of 7 Mc. and 10 Mc., giving a range of 27 to 30 Mc. It was found necessary to have a co-axial line connecting the receiver to the converter, and both receiver and converter completely shielded, to prevent pick-up of strong signals in the region of 7-10 Mc. However with all these precautions a few strong signals did appear at about strength 4. Another very strong carrier, picked up at 29.2 Mc. approximately, proved to be a harmonic of the receiver oscillator, which would have a very great nuisance value. The system also showed very uneven sensitivity due to

the output transformer of the Converter being untuned, whilst the first i.f. (the receiver) was varied. Attempts were made to broaden the resonance of this circuit by loading with a resistance, but this resulted in a marked decrease in the sensitivity of the Converter, although the circuit was broadened to the required amount. This same marked drop in sensitivity was also evident

when resistors were used to load the r.f. and mixer signal circuits, therefore it was obvious that the reduction in "Q," was bringing about a reduction in signal to noise ratio, because the tube noise was unaltered.

It was decided therefore that the best arrangement would be to use the conventional method of approach to the problem, and use the receiver as a fixed i.f. frequency, and tune the converter.

The remaining points to be decided were the choice of the first i.f. frequency, and the overcoming of the receiver oscillator harmonics falling within the bands to be covered. Actually these two problems are tied together to some extent, as by changing the receiver i.f., we also change the receiver oscillator frequency, and with it the position of its harmonics through out the high frequency spectrum. This problem was solved by considering what frequencies the receiver oscillator could be operated on, which would enable the harmonics to clear the bands covered by the Converter. As a first i.f. frequency of about 10 Mc. had been decided upon as being the best frequency for the Converter, a

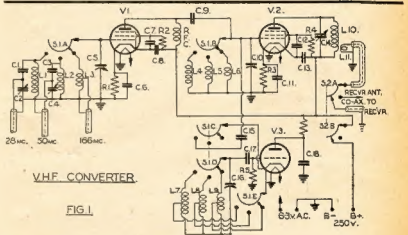

- C1, C3, C15—5 pF. Ceramicon.
- C2, C4—5-30 pF. variable.
- C5, C10—15 pF. variable with 2 rotor and 3 stator plates.
- C6, C11—0.001 uF.
- C7, C8, C12, C18—100 pF. mica.
- C9—50 pF. (N.P.O.) Ceramicon.
- C13—0.01 uF.
- C14—3-30 pF. mica trimmer.
- C16—15 pF. variable with 1 rotor and 2 stator plates.
- C17—50 pF. (N750)
- R1, R3—250 ohms wire wound resistor.
- R2, R4, R5—50,000 ohms.
- R6—30,000 ohms.
- S1a—e-3 bank 3 pole 3 position Ceramic wafer switch.
- S2a, b—d.p.d.t. switch.
- RFC—250 mH. r.f. choke.
- V1 V2—6AG5 peanut valves.
- V3—9002 peanut valve.
- L1—28 Mc. aerial, 10 turns 1/4" diam. 1/2" long, 18 s.w.g. enamel.

- L2—50 Mc. aerial, 6 turns 1/4" diam. 1/2" long, 18 s.w.g. enamel.
- L3—166 Mc. aerial, 1 1/2 turns tinned copper, 1 1/2" long overall with small "U" in centre 3/4" high and 1/4" wide, tapped at top of "U".
- L4—28 Mc. mixer, 10 turns 1/4" diam. 1/2" long, 18 s.w.g. enamel.
- L5—50 Mc. mixer, 6 turns 1/4" diam. 1/2" long, 18 s.w.g. enamel.
- L6—166 Mc. mixer, 14 s.w.g. tinned copper.
- L7—28 Mc. osc., 10 turns 1/4" diam. 1/2" long, 18 s.w.g. enamel, tapped at 3 turns from ground.
- L8—50 Mc. osc., 6 turns 1/4" diam. 1/2" long, 18 s.w.g. enamel, tapped at 2 turns from ground.
- L9—166 Mc. osc., 9 turns 1/4" diam. closewound, 18 s.w.g. enamel, tapped at 3 turns from ground.
- L10—9.545 Mc. i.f., 38 turns 1/4" diam. closewound, 29 s.w.g. enamel.
- L11—I.F. link, 3 turns 28 s.w.g. enamel.

*Technical Editor: 23 Parkside Avenue, Balwyn, Victoria.

few calculations showed that the following frequencies would be suitable for our receiver oscillator:—

Receiver oscillator 9 Mc.—3rd harmonic 27 Mc., 6th harmonic 54 Mc., 18th harmonic 171 Mc., and all other harmonics would clear the bands.

Receiver oscillator 10 Mc.—3rd harmonic 30 Mc., 5th harmonic 50 Mc., 17th harmonic 170 Mc.

Receiver oscillator 11 Mc.—3rd harmonic 33 Mc., 5th harmonic 55 Mc., 15th harmonic 165 Mc.

From the above figures it can be seen that if the receiver is set so that the oscillator is any of the above frequencies, oscillator harmonics will be either on the band edge or clear of the band. The decision was made to operate the receiver oscillator on 10 Mc., so that the harmonics could be used to mark the band edges, and therefore convert the harmonics from a nuisance into an asset.

If it is required to make the band edges with a great degree of accuracy, any receiver capable of tuning in WWV on 10 Mc. is used, and the receiver connected to the Converter varied until the receiver oscillator is heard to zero beat with WWV. This will mean the receiver is set up for a first i.l. frequency of 9.545 Mc. If the receiver has an i.f. of 455 Kc. and the oscillator is operated on the high frequency side of the signal frequency. As very strong signals are received on frequencies as high as 170 Mc., excellent band edge markers are available.

This attack on the receiver oscillator harmonic problem, is the simplest that the writer could find which would be 100% effective, as no amount of shielding or isolation reduced these signals to a negligible amount. The only method not tried was a low-pass filter, with a cut off point at 10 Mc. located in the co-axial line between the receiver and converter, because it was obvious from the tests that this line was carrying the harmonics to the converter. This method was discarded because it had been decided to install a switch in the Converter to connect the co-axial line from the receiver, either into the Converter output, or the normal receiving antenna, and any filter in this line would be in series with the receiving antenna when the Converter was not in use.

CIRCUIT After these preliminary experiments the circuit was drawn and the Converter built, and it was found that there were still a few problems to be overcome, so we will discuss these items whilst describing the circuit.

As can be seen from the circuit diagram in Fig. 1, three separate co-axial inputs are provided for each band, because at these frequencies, beams, ground plane, or vertical antennae would be used, each with its own individual co-axial line, thereby avoiding the necessity of switching the input circuits in the Converter. On 28 and 50 Mc. bands the co-axial lines are matched by a capacity network across the grid coil, and by varying the 3-30 pF. trimmers and the inductances, it is possible

to find values of each which will give the best signal strength for the antenna used.

This will indicate a correct match between the co-axial impedance and the impedance of the grid circuit. These circuits once set require no further adjustment. A similar system was tried at 166 Mc. but it was found necessary to load the grid circuit by tapping the co-axial line up the grid coil, to prevent the r.f. stage oscillating at this frequency. It was also found necessary to have cathode by-passes of 0.001 uF. in both r.f. and mixer circuits to prevent oscillation at 28 Mc. The screen and plate by-passes are connected to the other end of the cathode to that occupied by the cathode resistor and by-pass for in all v.h.f. tubes, the cathode is brought out to two separate socket pins. The plate of the r.f. stage is capacity coupled to the mixer grid circuit, as experiments showed this coupling to be just as effective as the separate primary winding at these frequencies, and it also simplified our switching. The output circuit of the mixer is tuned to 9.545 Mc., as mentioned previously, and is tuned by a 3-30 pF. condenser. The output link is brought through a co-axial line to a double pole, double throw switch, which connects the co-axial line from the receiver, either to the output of the Converter, or to the normal receiving antenna, which connects to a terminal on the Converter. The second pole of the switch, cuts the h.t. to the Converter when it is not in use.

The oscillator is a grounded plate Hartley and injection into the mixer grid circuit is obtained by taking output from the cathode tap, and feeding it through a small capacity to the mixer grid. The value of this capacity is altered by switch section 51c, as a value suitable for 28 Mc. is far too great for 166 and 50 Mc. Experiments showed that the capacity existing in the switch contacts gave the correct amount of injection, together with the pick-up from the lead running from the oscillator cathode tap into the mixer shield compartment, for 50 and 166 Mc. operation. On 28 Mc. this degree of coupling was not nearly great enough, so the small Ceramicon is switched in to overcome this.


It is opportune at this time to mention several difficulties which had to be overcome before correct operation of the Converter could be obtained. The first problem occurred on the 28 Mc. band, where the oscillator was operated on the low frequency side of the signal frequency, i.e. from 17.455 to 20.455 Mc. A bad case of double spotting occurred, the image occurring about 1 Mc. from the signal. Lack of image rejectivity of the receiver used with the Converter was suspected, but this did not prove to be the reason.

The true reason proved to be due to the following fact—with the converter oscillator on the low frequency side of the signal circuits, images would be received from stations twice the first i.f. frequency away, that is, from 7.910 to 10.910 Mc., which it will be noted, covers the converter output frequency, or first i.f. of 9.545 Mc. This meant that the Converter was receiving the signal in the normal manner, converting it to 9.545 Mc., and then the oscillator was again beating with this signal and re-converting it to the first i.f. frequency when the Converter was tuned away slightly from the signal frequency. Because this first i.f. signal existed in the mixer circuit, it can be seen that there would be no attenuation by the signal circuits (i.e. the r.f. and mixer grid circuits) which would make the image extremely strong. The remedy of course was simply to operate the oscillator on the high frequency side of the signal frequency for 28 Mc. operation.

On the 50-54 Mc. band the oscillator is operated on the low frequency side of the signal, and no trouble was encountered here.

The 166 Mc. band was tackled next, and it was found that the oscillator dropped out of oscillation at about 145 Mc. and could not be coaxed back. From about 120 Mc. the output of the oscillator had shown a decided dropping off in output, so it was decided to use the second harmonic of the oscillator, and run it in the region of 80 Mc. The output on the second harmonic was found to be greater than the fundamental when operated in this manner; that is comparing the output on the second harmonic of 80 Mc. against the fundamental on 145 Mc., which was as high as the oscillator would operate. In addition the oscillator was much more stable, and the all round performance of the Converter was now such, that the three bands tuned just as easily as the normal receiver on lower frequencies.

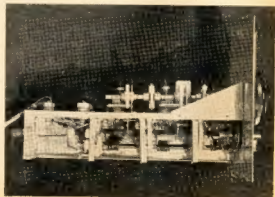LAYOUT Up to now no comments have been made on the physical layout of the Converter, although it is quite obvious that the success or failure of a unit of this kind is entirely dependant on it, particularly with band-switching. In case some of the components are not available to enable duplication of the original, it



would be as well to describe the method of setting out, so that the length of all leads will be at a minimum, in the circuits which require them to be that way, and it must be borne in mind that preference must be given to the highest band covered.

The three condensers were fitted with their flexible couplings, and laid out on the table, measurements were then made of the distance between the three bearings, thereby giving the distance between the front panel, and the following two mounting brackets for the condensers. The switch banks were then laid under the condensers, so that the switch connections are directly under their respective stator connections of the condensers, then allowing for the $\frac{1}{2}$ " mounting pillars for the switch banks, the distance between the shield divisions can be obtained. The actual width of the Converter is largely a matter of individual choice, as some may prefer to make the unit self contained, with built in power supply; however the distance from front panel to the dividing partitions must be exactly right if all leads are to be kept to a minimum.

In the illustration it will be noted that there are four main shielded compartments. The rear compartment contains the power input, co-axial inputs for the three bands, co-axial outlet to receiver, which is the rear outlet of the four, antenna terminal for receiver projecting from rear of Converter, air trimmers for 28 and 50 Mc. bands, and finally the d.p.d.t. rotary switch for changing the Receiver from Converter to receiving antenna.

The next compartment houses the r.f. stage, following which is the mixer compartment, with the output coil in the small shield above the chassis.

The front compartment, nearest the front panel, is the oscillator section of the Converter.

In Fig. 2 the drawing shows the essential components in the mixer compartment. The drawing has been made with the Converter in an inverted position, viewed from front to rear, and shows both a plan and elevation. In the plan view the pigtail of the condenser rotor projects through a hole cut in the chassis, and a heavy 14 gauge wire is soldered to the pigtail at this point and brought up in a curve to provide a point for the cold ends of the coils.

Another hole is drilled in the chassis, directly under the stator tie point, and the lead from there is brought directly on to the wiping contact of the switch

bank. The wire running from the No. 1 contact of the bank to the condenser pigtail, is the 166 Mc. inductance, for even with the reduction of lead length to a minimum, there is still sufficient inductance in the wiring and switch contacts to need only a straight wire to complete the coil. This fact does not appear to be detrimental to the operation of the circuit, as quite a reasonable peak in signal is obtained when the aerial and mixer circuits are tuned.

The grid pin on the mixer socket is located so that this lead is kept to a minimum. If a straight wire is not found to have sufficient inductance, it is advisable to use a hairpin coil here. The 50 and 28 Mc. coils are located where shown, with preference on shortness of leads given to the 50 Mc. band.

These coils are adjusted by holding a soldering iron at the point X, where they connect to the main 14 gauge supporting wire, and drawing the coils in and out, spring fashion, to obtain the correct inductance. Final tuning can then be done by slightly separating the turns of the coils with a screwdriver. These methods of coil adjustment, have

ment of the coils is made with the spreading and contracting of the turns by means of the screwdriver.

The steel rod which turns the switch banks was cut off near the clicker plate, and a piece of bakelite rod filed to replace it. This was done to remove as much metal as possible from the fields of the coils. The aerial change-over switch was also controlled by a bakelite rod, for the same reason.

The three variable condensers used were stripped down to give a large degree of band-spreading, and in the finished Converter the following ranges were obtained:—26.9 to 30.4 Mc., 49.9 to 55.2 Mc., 160 to 172 Mc. The oscillator condenser was reduced to one rotor and two stator, and the r.f. and mixer condensers to two rotor and three stator plates. With this arrangement of capacitors it was found that tracking was quite satisfactory on all bands.

ALIGNMENT One of the main problems associated with any piece of equipment such as this, is the problem of finding the band on these frequencies, particularly on 166 Mc. The 30 Mc. band is not so difficult and the 28 Mc. band quite easy with the activity now to be found there. Therefore it is advisable to get the Converter working on 28 Mc. first, following with 50 Mc. and then 166 Mc. The Receiver should be set to 9.545 Mc. as previously described, and the Converter output circuit peaked to give the greatest noise.

An Alignment Oscillator is then set to 28 Mc. and the 28 Mc. band set to the correct setting on the dial. If it is desired to cover the 27 Mc. section of the band, the Oscillator should be set to 27 Mc. and the oscillator coil in the Converter adjusted to bring the signal in at nearly full scale, then with an antenna attached the signal circuits are set for maximum noise, by peaking at the middle of the band. The 50 Mc. band is adjusted in a similar fashion, except that the Alignment Oscillator is adjusted to 25 Mc. and the second harmonic used to locate the band. With the Receiver oscillator set on exactly 10 Mc. as previously described the 50 Mc. point will be indicated by a strong signal being received from the 5th harmonic from the Receiver.

After these two bands have been set up, it is necessary to locate the 166 Mc. band. If a calibrated Wavemeter is available, it is only necessary to tune in one of the Receiver oscillator harmonics and then vary the Wavemeter until the oscillator pulls out of oscillation. The oscillator coil should then be altered until it pulls out at 85 Mc., which should then place the Converter on 170 Mc., as the second harmonic is used. A signal is then tuned in and with the three condenser couplings disconnected, each condenser varied to give maximum gain. It should be noted that it is necessary to connect an antenna during these adjustments, to avoid oscillation in the r.f. stage. Even a short piece of wire is all that is necessary. The frequency is finally checked by link coupling the Wavemeter in series with the

(Continued on page 7)

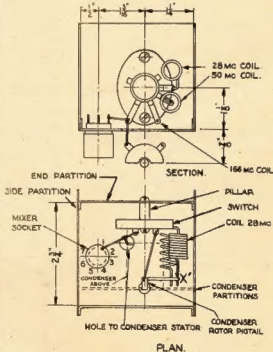


FIG. 2.

proved most effective, and it is surprising the large range of frequency over which the Converter can be varied.

The two side shields of the Converter are removed for wiring and adjustment of the coils in an approximate manner. With the shields in place fine adjust-

A Flextal Conversion Exciter Unit

(Courtesy Radio Publications Incorporated)

BY A. K. McLENNAN*, VK3AKM

This unit, of the variable frequency type, first made its appearance in "The Jones Radio Handbook," fifth edition.

The principle of operation is to beat a variable frequency against a fixed frequency and have the resultant "beat" frequency in a useful spectrum. Thus by having a fixed frequency of 4,300 Kc. and beating against it another, variable from 800 Kc. to 550 Kc., the resultant "beat" will be variable between 3.5 Mc. and 3.75 Mc. This will cover half the 3.5 Mc. band, more than twice the 7 Mc. and 14 Mc. bands, and all of the 28 Mc. band. This provides a very useful coverage.

In the unit to be described, the fixed frequency is obtained from a Pierce Crystal Oscillator, using a 6C5 triode, while the variable is from a Hartley type of self-excited oscillator, using a 6F6 as a triode. The beat frequency is obtained from the plate circuit of an 802, this tube being used as a mixer.

In the opinion of the writer, points in favour of this unit are:—

- 1—Stability of a self-excited oscillator is much easier to obtain on the comparatively low frequencies of the broadcast band than on the "Ham" bands.
- 2—When using the usual type of V.L.O. on a low frequency, each time the fundamental is moved 1 Kc., the operating frequency is moved by the amount of multiplication. With this unit the output is in the 3.5 Mc. band and moving the low frequency oscillator 1 Kc. only moves the "beat" frequency 1 Kc. This allows for very easy operation when one wishes to QSY.

The constructional details are not in any way complex, all that is necessary is to make sure it is a solid job, putting each tube and its components in a separate compartment, drill "breather"

holes in the top of the cabinet over each tube, with a shield around the 6C5 to the same height as the cabinet, and mount the voltage divider externally, so that there is a minimum of heating of the components. No voltage stabilizer was used in the writer's unit as it was not found necessary. A variation of voltage caused both oscillators to move in the same direction, in this case higher, with the result that the beat did not shift to any audible note.

This test was made using the fourth harmonic of the local b.c. station which is 3,320 Mc. and after allowing the heaters to "warm up" for ten minutes no frequency drift was noticed over a period of forty-five minutes.

A full point to point description of the construction will not be attempted here, as any person intending to build it will have sufficient knowledge to do so from the circuit.

Although not shown in the circuit it is a good plan to place a milliammeter in the plate circuit of the 802.

It will also be noted that there is no h.t. on the screen of the 802. This is quite in order as the screen is used purely as an injector grid.

If the suppressor were used there would be no shield between the injector grid and the plate and this would allow too much of the low frequency to appear in the plate circuit.

The writer has used one of these units for some months now and has found it to be very satisfactory. However there is one point, watch carefully the frequency of the Crystal used, making sure that it will not cause any harmonic of the Hartley to fall in the 3.5 Mc. band in close relation to the beat frequency.

Take the case of a Crystal on 4.68 Mc. When tuned for a beat frequency of 3.51 Mc. the Hartley is on 1,10 Kc. and its third harmonic is also on 3.51 Mc. This is alright if the beat is "dead on" 3.51, but between 3.5 and 3.51 a second signal appears and can cause a deal of trouble.

Crystals having fundamental frequencies between 4.3 Mc. and 4.5 Mc. are free from this trouble.


The tuning procedure is as follows:—

(1) Remove the 6F6, and using a Crystal in the 3.5 Mc. band tune the plate of the 802 to resonance. This ensures that the Pierce Oscillator is working and also gives an idea of where the "dip" should be when using the conversion Crystal.

(2) Replace the 6F6 and remove the 6C5 and with the aid of a b.c. receiver set the paddler of the Hartley until the frequency is 3.5 Mc. removed from the conversion Crystal, i.e. with a 4.3 Mc. Crystal set the Hartley on 800 Kc. Do this with the band-spread condenser at minimum capacity, because, as we are using the difference of the two frequencies the unit tunes "backwards," i.e. an increase in capacity results in an increase in the beat frequency.

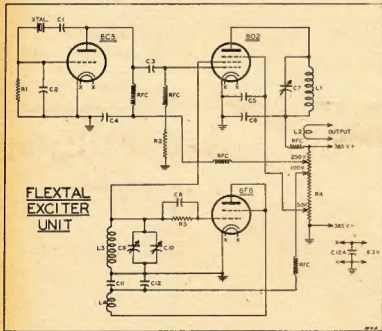(3) Replace the 6C5 and using the conversion Crystal check the band-spread with the aid of a frequency meter, at all times keeping the 802 plate at resonance.

The unit is then ready for work and has plenty of output; in fact, the writer



- C1—0.01 μ F.
C2, C3—100 pF.
C4, C5, C6—0.001 μ F.
C7—50 pF, variable.
C8—500 pF.
C9—385 pF. (broadcast).
C10—100 pF, variable.
C11—0.01 μ F.
C12—8 μ F.
C13—0.006 μ F.

- R1, R2—50,000 ohms.
R3—5,000 ohms.
R4—35,000 ohms.
RFC—2.5 mH.
L1—48 turns 22 gauge close wound, 1" diam.
L2—8 turns 22 gauge over cold end L1.
L3—Broadcast coil third of turns removed.
L4—30 turns 28 gauge, sliding over L3.

*Assist. Engineer Station 3UL; Landsborough Road, Warragul, Victoria.

had difficulty in reducing drive sufficiently when driving an 807 on 3.5 Mc.

If there is any doubt about not using voltage regulation on the Hartley, a VRI05/30 may be used.

It is the intention of the writer to make this unit a real "Flexial" by incorporating a switch to bring several spot Crystals in, thus having an exciter unit which will be quite versatile.

Before finishing may I be allowed to write a word of advice:—

There has been, lately, some talk about v.f.o.-itis, i.e. running up and down the band and thereby causing quite an amount of unnecessary QRM. Take a tip, and incorporate a switch that will allow the "Flexial" to be brought on independently of the final. This will allow of "netting" without causing QRM.

Band Switching Converter

(Continued from page 8)

antenna lead, and with a signal tuned in, a point will be found on the Wave-meter dial where the incoming signal dips suddenly. If Converter is operating on its correct frequency this should be on the 166 Mc. band. The lead lengths are then adjusted to give alignment.

Another method of finding the 166 Mc. band is by the oscillator harmonic method. This requires an Alignment Oscillator covering the range 15-30 Mc.,

and the principle of operation is as follows:—The Converter is tuned to a 10 Mc. point, which is one of the Receiver harmonics, and the Alignment Oscillator frequency is varied until a beat is heard with the signal tuned in on the Converter, this frequency is noted. It will be found that in the range 15 to 30 Mc. quite a few points will be found. By referring to the table below, the frequency to which the Converter is tuned will be found above the vertical column of frequencies which agree with the points noted on the Alignment Oscillator. It is important that this check be made only after the signal circuits have been aligned, otherwise images will be loud enough to be confused with the signal.

The table only shows frequencies over a limited range, but can be extended by simply dividing the frequencies in the top line by the harmonic required, such as 5, 6, 7, etc. Also the table is not calculated to a high degree of accuracy as this is not necessary to locate the band.

70	80	90	100	110	120	130	140	150	160	170
23.3	26.7	30	25	27.3	30	26	28	30	26.87	28.4
17.5	20	22.5	20	22	24	21.6	23.38	25	22.9	24.3
14	16	18	16.7	18.4	20	18.6	20	21.4	20	21.22
		15	14.3	15.8	17.15	16.25	17.5	18.7	17.8	18.9
					15	14.45	15.5	16.7	16	17
								15	14.55	15.45

In operation the Converter has proved to be an excellent performer, and it has retained its calibration on all bands, whilst the convenience of switching bands has to be experienced to be appreciated.

TECHNICAL EDITOR'S NOTE

It is regretted that owing to the indisposition of one of our draughtsmen, an article on the SCR522 Conversion, scheduled for this issue, was not ready in time for publication.

This article, which will appear in the April issue, should appeal to all Amateurs who are interested in conversion of service equipment.

From correspondence received, it is obvious that articles of this nature are extremely popular, and it is hoped to publish a series covering equipment now available on the Australian market.

Any suggestions, data, or conversion material our readers may be able to supply, will help to keep this section of the main technical presentation complete. It is up to you to keep the ball rolling.

VEALLS offer a New, Improved Oscillator!

The UNIVERSITY

Vealls offer the outstanding new Model X.O.A. A.C. operated OSCILLATOR, the very latest triumph of the famous "UNIVERSITY" series! Especially suitable for the alignment and general testing of receivers. Moderately priced at Vealls at £17, (plus sales tax).

KINGSLEY K/59'er SIGNAL BOOSTER

Since its recent introduction the K/59'er has met with widespread favour, many hundreds now being used throughout Australia. The K/59'er does everything claimed of it, and is being acclaimed everywhere by satisfied users. It operates on 10 metres, and additional plug-in coil boxes to operate on the 6 and 20 metre bands are now available at little extra cost.

VEALLS

Estab. 1911

243 Swanston Street, Melbourne. Phone: FJ 3145
299 Chapel Street, Perth. Telephone: LA 1605
Mail Orders: Box 2141T, G.P.O., Melbourne.

And here are a few more Special Snaps from Vealls!



★ LEXINGTON PICK-UP

VEALLS bring to you this new revolutionary-type English marving coil pickup, giving full reproduction of the total audio frequency range!

Price: Senior Model, £15/2/6. Standard Model, £17/6/6

★ TRANPRO VALVE AND CIRCUIT TESTER.
For A.C. and Vibrator operation, £32/19/6.
plus Sales Tax

GRID DRIVE

One important question that is sure to come up in the design of a new transmitter is how much power is needed to adequately drive the individual stages. Tube manufacturers have set up driving power figures in typical operating data, but, unless this information is interpreted correctly, the driver stages may be underdesigned. Here is an analysis of grid driving power as listed in tube operating data which is reprinted from R.C.A. "Ham Tips," Vol. VII, No. 3, 1947.

At higher frequencies consideration must be given to r.f. and transit-time loading losses. If the stage in question is to operate above 30 Mc., it is advisable to provide 3 to 10 times the published low-frequency driving power figure in order to insure sufficient drive plus a reasonable margin for safety.

After the design has been crystallized and the transmitter constructed, tests and adjustment should be made to insure that the stages are being properly driven. If, as in many cases, an amplifier tube is to be operated with conditions differing somewhat from those published under a set of suggested typical operating conditions, the performance can be checked as follows:—First, load the amplifier to the desired value of plate current. Then vary the grid current slowly (tank circuit tuning remaining unchanged) and note the change in output.

If the change in output is roughly proportional to the change in grid drive, the stage is underdriven. Grid drive should be increased until very little increase in output results from a large increase in drive. Under this condition, the stage is said to be saturated. Of course, the maximum rated value of d.c. grid current should not be exceeded.

The penalties for an underdriven stage are low power output, low efficiency, and, if the stage is plate modulated, severe distortion at high levels of modulation. The latter condition will readily be recognized as downward modulation, and, if a pure sine wave is used for test, a decrease in average plate current will be noted as the modulation level is increased.

CORRECT GRID DRIVE IMPORTANT

It is very desirable to saturate amplifiers, especially those driven by a series of frequency multipliers. This comes about because it is rarely possible to saturate frequency multipliers and to stay within tube ratings. Consequently, a small decrease in supply voltage on the multiplier stages may cause a large decrease in grid drive and in output of the final amplifier stage. It is important, therefore, that the amplifier grid be saturated so that full output is maintained regardless of variations in supply voltages.

It is possible to overdrive as well as underdrive tubes. However, overdrive occurs rarely. There is little to be gained by over-driving and something to lose. Although there should be no actual damage to the grid or cathode unless the maximum ratings for d.c. grid current or d.c. grid bias are exceeded,

over-driving can cause excess harmonic radiation and low power gain.

Over-driving a beam tube or pentode may cause the screen grid to be overloaded before the control grid. This condition may be checked by metering the screen current to determine whether the screen input is within ratings. Adjustment of both bias and screen voltage may be necessary to allow the tube to be properly saturated and still remain within screen input ratings.

The correct amount of grid drive is an important detail of power tube application. With other conditions properly maintained, it insures high power gain, high plate efficiency, and long tube life.

The value of driving power shown in tube data bulletins includes only the actual power input to the grid plus the power lost in the bias supply. It does NOT include r.f. losses that occur in the tube, tank circuit, socket and wiring, or losses in the tubes, caused by transit-time loading.

It is not feasible for the tube manufacturer to give total driving power figures because there is no way of anticipating conditions under which the tubes will be used. Grid power requirements will vary considerably even in well-engineered designs, and the extreme ranges are quite large. It is better, therefore, that printed specifications indicate only the sum of grid power and bias losses.

Because the driver tube must supply all the losses between its plate and the grid of the driven tube, these losses must be added to the figure given in the tube data for driving power requirements. On an average, in the frequency range up to 30 Mc., the losses are large enough to indicate the choice of a driver tube which has a rated output of about twice the grid power rating of the driven tube.

Driving-power measurements are usually made at 100 Kc.—where r.f. losses in the tube are negligible—by measuring the peak r.f. grid voltage (Eg) and the average grid current (Iav). Then, the relation $Wd = 0.9 Eg Iav$, gives the driving power in watts. This is the figure shown in tube bulletins.

TO WHOM IT MAY CONCERN

Two manuscripts have been received signed by "Old Hombre" and "Vieille Femme." Would the person concerned be so good enough to furnish me with his correct name and address (which is not for publication), after which I can possibly make use of the contributions. —Editor.

CALCULATING DISTANCE OF QSOs.

By F. S. DAHL*, VK7KA (Portable)

Now that v.h.f. and u.h.f. DX is being achieved, it seems interesting to know somewhere close to the mileage achieved in a contact. This can be done simply by trigonometry, and the following method gives reasonable results without recourse to involved data on the oblate spheroid shape of the earth, to the convergence of meridians and the eccentricity of geodesics.

Firstly know your QTH. This can be had by scaling latitude and longitude of your shack from a large scale local map or district survey chart. Since maps are readily available at scales of at least 1" to the mile, a position can easily be fixed within say 15 seconds of arc, which is about $\frac{1}{8}$ mile. One minute of arc approximates 1 nautical mile—1.1515 statute miles.

Now suppose Ham A in Adelaide works B in Melbourne. The Cosine of the arc on the earth's surface in degrees and minutes equals the sum of two terms.

Firstly, Cosine Latitude A \times Cosine latitude B \times Cosine Difference in longitude, written—

Cos. lat. A \times Cos. lat. B \times Cos. diff. in longitude.

The second term is:—

Sine lat. A \times Sine lat. B.

Perform these two multiplications then if both stations are on the same side of the equator, add the answers together. This figure is the natural cosine of the angle subtended at the earth's centre by the arc on the earth's surface joining the two stations.

Convert this angle into minutes and this gives nautical miles the stations are apart, and finally multiply by 1.1515 to arrive at statute miles.

If the stations are on different sides of the equator, then subtraction of the terms is necessary. The lesser from the greater.

The following is a worked example:—

Latitude Adelaide S 34° 53' 33"

Latitude Melbourne S 37° 49' 53.5"

Difference in Longitude 6° 23' 27.5"

The first term Cos. lat. Adelaide \times Cos. lat. Melbourne \times Cos. Difference in Longitude

Cos. 34° 53' 33" \times Cos. 37° 49' 53.5" \times Cos. 6° 23' 27.5"

= 0.816994 \times 0.789819 \times 0.993786

= 0.643544 using natural cosines.

The second term, Sine latitude Adelaide \times Sine latitude Melbourne

= Sine 34° 53' 33" \times Sine 37° 49' 53"

= 0.572516 \times 0.613340

= 0.351147

Add these two results together—

0.643544 + 0.351147 = 0.994691.

Now in your 'big' tables look up what angle has a natural cosine of 0.994691, and we find 5° 54' 20" which equals 334.333 minutes. Thus the points taken

(Continued on page 9)

*Lands and Survey Dept., Tasmanian Govt. Service, Box 641D, Hobart.

WRITING AN ARTICLE FOR "AMATEUR RADIO"

It is the purpose of this article to give some "dope" to you, on how to impart your knowledge to your fellow Ham via the medium of "Amateur Radio."

In order to have a magazine, it is evident that editorial material be obtained. Naïve as it seems, that statement carries plenty of meaning, and is not facetious as it may appear.

We like to receive articles with a basically good idea and which usually can be sent to the printer without a mark (correction) on them. But if the idea is good, we will re-write it if necessary and make it suitable for publication.

Out of ten articles received, for instance, there may be three, four or five which are acceptable as they are written (with the exception of some grammatical and technical corrections or clarifications). Occasionally the prize of them all pops up, an article which has been well written, technically and grammatically sound, and—of all things—with a subject that will be of great interest to the majority of Hams, as well as being technically hot. Yes, this sort of article is a rarity, but all connected with the magazine find it fascinating, because we never know when such a prize will show up.

The following remarks are representative of our collective sins as would-be writers:—

1. We type our manuscripts with no extra spacing between lines and/or with

little or no margins between the writing and the edges of the sheet. Manuscripts should be typewritten, if possible (or legibly written), on paper approximately 8" x 5½", with at least 1½" margins, and double spaces between lines. When the article is written, get the XYL to read it out aloud, you will see at once if it has continuity, and is legible to a person other than yourself.

2. We forget to send one or more pages of the manuscript.

3. We overlook the little matter of writing our name and the title of the article on each sheet of the manuscript, very important if the pages should become detached.

4. We fail to number the sheets consecutively, and sometimes place the sheets out of reading order.

5. We fail to include all constants in the wiring diagram. Draw the schematic clearly, mark all constants, don't worry about making a copper-plate drawing, our draughtsmen will do that for you; they know what is required by the block-makers.

6. We send a print taken on a small camera. A reasonable size print is required for blockmaking. If possible send the negative and advise if you want it returned.

THE SUBJECT

Of greatest importance is the subject, if it is a piece of equipment, expressed for the man without a.c. power, that is acceptable. Many Hams have to use

battery power in Australia. The conversion of a piece of commonly available ex-service equipment, a new antenna, receiver, or some transmitting gear, v.h.f., apparatus—the subjects are too numerous to mention.

The whole thing is so simple; merely sit down and think of what you did first in constructing your equipment or whatever it is. Make a few notes. Then write all about it. Take up the second step and write all about it. If there's some connecting point between the two, as there usually is, write it in the second step so as to make a logical connection. Proceed likewise until your story is finished. That's all there is to it. Let the Editor worry about "polishing up" the continuity of composition.

Calculating Distance of QSOs

(Continued from Page 8)

in Adelaide and Melbourne are 354 333 nautical miles apart. Multiply this by 1.1515 and we have 408.01 statute miles.

Reworking the above example by recourse to Napier's Analogy I got 408.07 miles and by vigorous application of the meridional distortion of the earth's surface and the convergence of meridians, the true figure of 408.0517 miles is obtained.

It appears to the writer that some standard formulae should be adopted for arriving at the distances likely to be claimed in v.h.f. and u.h.f. work and the above formulae presents itself in that it is easily followed and worked

POWER TRANSFORMERS

The reliable quality and uniform performance of Trimax have meant an ever-increasing demand by users everywhere, including the P.M.G.'s Department, Broadcasting Stations and leading experimenters. This recognition has resulted in temporary shortages which our production has not yet overtaken.



by TRIMAX

29-30 FLEMINGTON ROAD
NORTH MELBOURNE, VTC

<p>Interstate Representatives:</p> <p>NSW: L. B. Graham 5 North York St SYDNEY</p>	<p>QUEENSLAND: Chandlers Pty Ltd Cnr. Albert and Charlotte Sts. BRISBANE</p>	<p>S.A.: C. N. Muller Warrendale Buildings Greenfield Street ADELAIDE</p>	<p>W.A.: R. D. Benjamin, 197 Murray Street, PERTH</p>	<p>TASMANIA: W & G Genders Ply Ltd, 53 Cameron Street, LAUNCESTON</p>
--	---	--	--	--

INQUIRE FROM YOUR NEAREST SUPPLIER

HAM RADIO SUPPLIERS

18 SWAN STREET, RICHMOND

AMATEURS AND RADIO EXPERIMENTERS, SEE US FOR ALL YOUR RADIO REQUIREMENTS.

WE HAVE A VERY LARGE AND EXTENSIVE RANGE OF SHORT WAVE EQUIPMENT.

A NEW SHIPMENT JUST ARRIVED. ALSO LARGE CONSIGNMENT OF VALVES OF ALL TYPES, including:—807, 6J7, 6V6, 6B8, 6U7, 6K8, 6J8, 6SH7, 6AC7, 9002, 9003, 954, 955, 956, 5V4, 5YB, 6X5, VR105, VR150, 9072, 1603, 879. ALL TYPES OF 2-VOLTS AND 1.4 SERIES.

SPECIAL DISCOUNT GIVEN TO HAMs.

COMPARE OUR PRICES

OSCILLOSCOPES R.A.A.F. Indicator units fitted with 5" C.R.O. Tube, also using 6—1852's and 3—6H6 Valves. Gain, Bias, Focus and Range Controls. The units and components are Brand New, but have no power supply. OUR PRICE, £8.

AMERICAN R.C.A. 8-valve Receiver, model DZ2. Covers broadcast and long-wave frequency. 750 K.C. to 32.5 K.C. Less Power Supply. Sacrifice at £25.

HIGH FREQUENCY RECEIVERS. Types AR301 and 46AAT. Covering 2½-6 metres. Valve line-up, 5 tubes, 955-956 Mixer stage—4-6A-C7's, 1.F. Stage, 2 Meg., 5V4. Rectifier. Power Supply, &c A gift at each. £15

TRANSCEIVERS, AMERICAN TYPE. S.C.R. 522 Tube line-up. Receiver 1—9002, 3—9003, 1-12J5, 1—12CB, 1—12AH7, 3—12SG7, Xmitter tube line-up, 1—6G6, 2—6SS7, 3—12A6, 2—832, 4 Xtal controlled channels in Xmitter and Receiver in 100-156 Mc/s Band. No xtals. Phone M.C.W. 9 Watts Output. Complete with Power supply, generator type, 28 volts D.C. input. OUR PRICE, £12/10/-.

COILS, plug-in type, for Australian and English AR14 Receivers, 25/- box or 1/6 each. Order now while supplies available.

VALVES.—We have large quantity of all types of Valves. Transmitting and Receiving.

TELEPHONE SWITCHBOARDS. 10 line. Good order, from £3 to £12 each. The Units have many uses on farms, &c.

AERIAL COUPLING UNIT. AT5-AR8. Matches 100 ohm link to any length or type of Aerial. Complete with 12 volt Relay and R.F. Meter. OUR PRICE, £1/10/0 each.

AMERICAN TYPE C.R.V. 52233. 6 valve, covers 40 and 80 metres Bands. Valve line-up, 2—6N7's, 1—807, 1—VR150 into 2—815's. Two slide in Coils. Phone M.C.W., C.W. An excellent buy at £10, less power supply.

OSCILLATOR. 75 meg., complete with output meter, very elaborate, 230 A.C. operated £25

HIGH-FREQ. TRANSMITTERS and OSCILLATORS.

We have in stock several of these units, which may be useful to high-freq. experimenters. Also have a quantity of incomplete units for wrecking purposes.

AMERICAN TRANSMITTERS.—20-watt Plug-in band type, CBV 52063A. Phone or C.W. valve line-up, 2 89's into 2 837's. RF meter, &c. Limited quantity only £20

REMOTE CONTROL UNITS, complete with mic. and phones. Morse key. Can be used for house phones, &c. Condition as new. To clear £1 each Order now.

EARPHONES.—Several types, including crystal, moving coil, magnetic. U.S.A. Navy types, with large ear pads. 35/- to £3 per pair Limited quantity only.

TRANSCEIVERS, 109's, S.T.C., 9 Valves, covers 80-metre band. Tube line of Receiver, 6U7's, 6K8's, 6B6's. Transmitter, 3-807's. Receivers easily convertible for local reception, 6-volt Vibrator operated. Price £12/10/0

TRANSMITTERS.—Famous A.T.5 50-watt, phone or C.W. Xtal or V.M.O. Tube line-up Occ. 6V6, Doubler 807, 2-807 in parallel in final. Band coverage 500 K.C.—15 Mc. Meter covers all stages. Input 12-volt A.C. or D.C. M.T.500-V-300. Generator supplied with unit, or A.C. Transformers and chassis supplied. Also Aerial Coupling Unit Price £25

TRANSMITTERS. 3B.Z. A.W.A. Xtal controlled, 6 holders, band coverage 3.5 Mc. and 7 Mc. Tubes used, 4-6V6's-1-807, Vibrator operated off 12-volt battery. Meter for all stages. This set operates on phone of C.W. Price £17/10/0

TRANSMITTER. American type, BC-191-E, 100-watt, phone or C.W. Precision built. Plug-in band change coils. Very elaborate power supply, adjustable filament and H. tension voltages, circuit breakers, relays, &c. A beautiful job: a welcome addition to any ham shack. Price £75

METERS.—All types. R.F. Thermo Couple, 0 to 1 A.M.P., 15/-, D.C. Milliamps 0 to 300 Mill., 15/-

FILTER CHOKES AND CONDENSERS, RESISTORS, VARIABLE AND FIXED.

Inspect all these items at

HAM RADIO SUPPLIERS

18 Swan Street . . . Richmond

Phone: JA 2584

After Hours: Haw. 4465

SPECIAL ATTENTION GIVEN TO COUNTRY MAIL ORDERS.

SUCH NICE PEOPLE

Victorian Divisional Council has ruled that the material contained under this heading must in future be signed by the person responsible for the writing. I, as Editor, feel that at least "Grem-lin" is entitled to make a statement, that I should justify my action in publishing the articles written by "Grem-lin," and further, that the two people, who in the first place were responsible for "Grem-lin's" appearance, should be permitted to defend their action.

I am aware of the identity of "Grem-lin" and suffice to say that his personal integrity is of the highest, his technical ability cannot be challenged, and his writings were inspired by a sincere attempt to clean up Amateur Bands.

Thomas D. Hogan, Editor.

"GREMLIN'S" STATEMENT

Editor, "A.R.",
Sir,

I understand you have been instructed by Council, Victorian Division, to publish my discourses under my call sign. I cannot agree to this for I firmly believe the article would no longer have the same value—however small—in this form.

Technically, I suppose you cannot accept this for publication minus call sign, but I'm sure Council will grant me the opportunity of saying "Au-revoir."

I am told several people have been greatly offended by my writings. To them I most humbly apologize, assuring

you that at all times I criticised various signs, having in mind nothing more than an earnest endeavour to assist in maintaining the high Amateur standard, in V.K. At no time were my remarks intended to be construed as personal r-fections.

Council, in their wisdom, issued this directive with, I believe, the thought "would 'Grem-lin' have the courage to come out into the open?" To my mind, it is not a question of my courage, but one of satisfying the desire of the majority of members. With the ball prettily knocked back into my court, the directive by Council has diplomatically gared the objective—exit yours truly.

Remembering my fore-runner "QRZ" I now silently steal back into the shadows, thanking Hams, one and all, for what to me was a happy association. Especially I thank those many friends who have written words of thanks and encouragement even though many have "had a mention." I have enjoyed it, for I feel I got to know more chaps than when I was a DX chaser.

Cheers and good hunting,

"GREMLIN"

Editor "A.R."

We were surprised, in fact astonished, to hear that Council had issued a directive which prohibits further publication of "Such Nice People" unless the real name or call sign of the author is published with it.

We have since had from the President the basic reason for Council's action, and we believe that "Grem-lin" has been victimised. We further believe that a

fuller inquiry into the matter would reverse the decision made by Council.

As you know we originally vouched for the character, integrity and the technical ability of "Grem-lin."

"Grem-lin" will not continue his notes unless under a "non-de-plume." He is not contemptuous, deceitful, insincere, vindictive, or facetious.

His notes if published conditionally, as required by Council, would lose their "news value" for we believe an overwhelming majority of readers first turn to "Grem-lin's" column when "A.R." comes to hand. No doubt, as Editor, you are aware of this fact more than we are.

May we ask that you use every endeavour to have Council re-consider the subject, for we believe that the majority of readers desire the continuance of these articles in the magazine.

Assuring you of our support, together with that of many amateurs with whom we have spoken on the subject of "Such Nice People,"

Yours etc.,

HARRY KINNEAR, VK3KN

ARTHUR EVANS, VK3VQ

ANNOUNCEMENT

Interstate visitors are invited by the Victorian Division to avail themselves of the services of the Administrative Secretary, Mrs Cross, who will furnish suitable introductions and information if requested.

When in Melbourne call at 191 Queen Street, or ring FJ 8997.

SUBSCRIPTIONS arranged to any Magazine or Paper throughout the World

RADIO—

Audio Engineering	£1 6 0
Communications	£1 2 0
C.Q.	£1 2 0
Electronics	£4 17 6
F.M. and Television	£2 0 0
Proceedings of the Institute of Radio Engineers	£3 19 6
R.S.Y.	£1 7 0
Radio Craft	£1 2 0
Radio News	£1 12 0
Service	£1 2 0

AMERICAN

SCIENTIFIC AND PHOTOGRAPHY—

Popular Science	£1 3 6
Popular Mechanics	£1 3 6
Mechanix Illustrated	£1 2 0
Scientific American	£2 0 0
Science and Mechanics	£2 15 6
Science Digest	£1 8 6
American Photography	£1 6 0
Camera	£1 18 0
Popular Photography	£1 6 0
U.S. Camera and Travel	£1 6 0

ENGLISH

Electronic Engineering	£1 12 6	Wireless World	£1 5 0
Practical Wireless	£2 9 0	Wireless Engineer	£2 0 0
Short Wave Magazine	£1 5 0		

AUSTRALIAN

Amateur Radio	£2 6 0	Radio and Hobbies	£2 6 6
Australian Radio World	£2 10 6		

VERY LARGE RANGE OF TECHNICAL BOOKS ON ALL SUBJECTS.

WRITE FOR LIST ON THE SUBJECTS YOU ARE INTERESTED IN.

McGILL'S AUTH-NEWS AGENCY

Established 1930.

183-85 ELIZABETH STREET, MELBOURNE, C.I., VICTORIA.

(The G.P.O. is opposite).

TELEPHONE: C. 8113-4.

VK4WI

The Transmitters and Receivers pictured here are operated by the Queensland Division of the Wireless Institute of Australia under the call sign of VK4WI. The persons responsible for the planning and construction of the station are to be congratulated on the completeness of the gear.

The use of three simultaneous channels for transmission of official broadcasts gives the Queensland Division the widest possible cover for the dissemination of its Divisional news.



The transmissions of the official Queensland W.I.A. station are probably well known to most VK4s and possibly to most VKs. Established in its present form shortly after the present Council started operations, it took over after the original set-up provided by VK4HA, and at present under the control of VK4FN it operates on the following frequencies simultaneously: 7100 Kc., 14342 Kc., and 52004 Kc. The station commences operation at 0900 hours each Sunday morning when members are invited to join in the usual round table discussion on current topics and items of news. The news for the preceding week is broadcast at 0910 hours, after which the hook-up takes place, and in all nearly 30 members have at one time or another taken part in the proceedings including several

VK2s. Frequency measurements are provided on nights specified in the Sunday broadcast, and this service is widely used according to operator VK4FN.

As you've probably been wondering what's behind the panels, a description of the station follows. The left hand rack starting from the bottom contains bottom three panels are power supplies, panel with single knob, the modulators, meter panel; 7 Mc. exciter comprising 6F6 oscillator and 802 buffer link coupled to an 813 with 100 watts input.

The centre rack, again from the bottom is d.c. power supply for relays; two racks containing power supplies; a Jack Field; Power Distribution Panel for 14 Mc. transmitter; Relay Panel; Power Distribution for 7 Mc.; an 27 Mc. f.m.

exciter, c.r.o. unit; Modulation Meter.

The right hand rack contains the 14 Mc. equipment. In the usual order; bottom 4 panels, power supplies; Modulator Panel; 14 Mc. exciter made up of 6CS, 6N7, 807 driving an 808 p.a. with 100 watts input.

The antennae used are Verticals, mounted on the one pole. The 50 Mc. transmitter, not shown in the photo, is a DR106, a trans-receiver using a pair of 807s in the final; receiver is a super-het. It is hoped that the next time you listen to VK4FN doing his stuff over this fine set-up you at least will know something of what's going on. The receiving position is self explanatory except to add perhaps that the meter under the Microphone is a power level indicator.

PLATE MODULATING THE BEAM TETRODE

BY E. A. CHARLES, VK5YQ

The good book recommends either feeding the screen via a dropping resistor from the modulated plate supply OR the use of a separate winding on the modulation transformer. Your attention is directed to another method that appeared in an advertisement by Emac (valve manufacturers) in QST, May 1947. Here the screen is fed via an audio choke (10 henrys or more) from a fixed supply (say, your exciter voltage

supply or from a voltage divider network on the main h.t.).

The screen is then "automatically" modulated because of normal variation in screen current under plate modulation.

It then becomes a simple matter to run the tube(s) at the correct—manufacturers'—ratings. With excessive (or absence of) drive your screen current/voltage doesn't go off on disastrous excursions.

The writer uses a Japanese 8 henry 30 mil. choke in the screens of push-pull 807s (with the usual 100 ohm re-

sistors and 0.001 uF. condensers). When originally tried with a single 807, the same amount of audio was required for a given r.f. input for 100% modulation (on the c.r.o.) as when using the screen dropping resistor. However, a slight increase in antenna current was noticed (antenna was a full-wave voltage-fed zapp) using the choke method.

Your attention is called to two necessary precautions. Firstly, arrange the switching so that the screen voltage is never on without or before the plate voltage; and secondly, on c.w. it is necessary to short out the choke.

Amateur Radio, March, 1948

You'll Build a **BETTER** Station . . . on an **EDDYSTONE** Foundation!

Type 533



Transmitting

Type 137



Condensers

Overall Dimensions (excluding Spindle) - Cat No. 137. — 42" long (less spindle), 3 9/16" wide, 2 1/2" high. Maximum capacity 60 pF per section (30 pF overall). Flash-over voltage, 2,000 R.M.S. (Air Gap .068 ins.) £5/8/5
Cat. No. 533. — 7 1/2" long (less spindle), 4 1/2" wide, 3 1/2" high. Maximum capacity 100 pF. Flash-over voltage, 4,500 R.M.S. (air gap, 2") £7/8/9

Adjustable INSULATED BRACKET

A strong bracket for mounting components which are controlled with a flexible coupler, extension spindle, etc. The insulated portion, which is made of DL9 material, is adjustable to give mounting hole centres of from 2 1/2" to 3 1/2" above the chassis. The hole size gives 7/16" clearance. The metal one-piece slide is finished

brown and fixes to the chassis by means of two screws

Cat. No. 1007 4/7

SLOW MOTION DIAL

Slow Motion Dial fitted with vernier reading device 3 1/2" diameter scale and large fluted, instrument knob. Reduction ratio, 10-1. This model is finished in matt black with white fillings.

Cat. No. 594 2/7




Contact your distributor **NOW** for a complete Price List of Eddystone Components

DIRECTORY OF DISTRIBUTORS

- VICTORIA: J. H. MAGRATH & CO.
208 Little Lonsdale St., Melbourne
- WEST AUST: CARLYLE & CO.
Hay St., Perth & 397 Hannan St.,
Kalgoorlie
- N.S.W: JOHN MARTIN PTY. LTD.
116-119 Clarence St., Sydney
- S.A: GERARD & GOODMAN LTD.
192-196 Rundle Street, Adelaide
- Q'LAND: CHANDLERS PTY. LTD.
Cnr. Albert & Charlotte Sts. Bris.
- TAS: W. & G. GENDERS PTY. LTD.
53 Cameron Street, Launceston

Australian Factory Representatives:

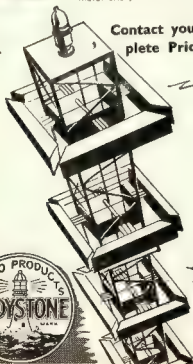KEITH HARRIS & CO. PTY. LTD. 51 WILLIAM ST., MELB. Tel. MB2119



EDDYSTONE OFFERS YOU
THE LATEST, MOST DEPENDABLE
COMPONENTS for FM., AM., & PULSE

Compiled by VK3QO, to whom all contributions can be sent

The last V.A. section meeting of the VNA Division was held on 28/1/16 and was well attended. In the absence of JNP, V.A. officer, due to Melbourne, the chair was taken by Divisional President, EVM, and the lecture was a very excellent one by Chas Higgins (SAID) and Alex Stevens, both of whom have been working in the VNA section in connection with the moon radar experiments. Everyone present was quite surprised at the amount of calculation (both astronomical and otherwise) which was necessary before this project was finally put into action. The VNA section is now being represented by EBE, SADI, SOO and SHU who, once they have completed the long trip down South by road. Other visitors

During Xmas holidays RYL-SUS (Rex and his XYL Gwen) took their portable to Ballarat and district and worked everything on the bend. Tx was 6VS 0.4a, lnto 6VS p.a.; Rx was 6000 ASTJ G0B; 4 wata loop. Later they moved to Tallourn where they worked 2BE. SALS drove them to a hill outside Tallourn where a CD noted 5G1 which was 3AL a bit surprised. 3HE, 3AKN, 3HE and 3AL were on the way home the way home where 3AKN and 3HE mobile.

"Ray Jones" outburst on page 21 of February A.E. concerning 80 Mc. "defect wacky verbiage" calls for answer. There is far less "tripe" on 80 Mc. than on the lower frequency bands as the boys are too busy discussing special v.h.f. problems; the fact that Ray listens on 50 Mc. proves this. "Absence of c.w." is most probably due to his Rx. which (by rumor) is a "rubber"!! ERO. 8CP. SPC.

(Continued on page 23)

lation, 19/6 each.

Federal President.—W. R. Gussow, VK3WG; Federal Secretary.—W. T. S. Mitchell, VK3UM, Box 2611W, G.P.O., Melbourne.

Zone Correspondents.—**Newcastle:** E. J. Baker, VK2FP, 13 Skilton St. Hamlyn Newcastle; **Coalfields and Lakes:** H. Hawkins, VK2YL, 27 Comfort Ave., Coorook, Western; G. J. Russell, VK2QA, Canonba Street, Nymcan, South Coast and Tablelands; L. H. Vale, VK2ANh, Box 73 Bega, Southern; E. N. Arnold, VK2QJ, 673 Forrest Hill Ave., Albany.

VK3BM, Quambatook, Western: C. C. Waring.
VK3YW, 12 Skene St, Stewartsburg, South Western:
B. Sactrine, VK3BI, 17a Raglan Street North,
Balarat, North Eastern: D. Facey, VK3DW, 18
Harold St, Shepparton.

VK7WI.—Second and Fourth Sundays at 103 hours EST on 7174 Kc. No frequency checks are available.

Cromwell St Battery Point Hobart
Northern Correspondent.—C. P Wright, VK7LZ,
Knight St Launceston

any person, executive, anyone knowing of any name not included on the above list or errors thereon should communicate with F.E. at the earliest.

At its 1947 Annual Federal Convention, the WIA directed its Federal Executive to approach I.A.R.U. and "seek international member-society comment on the desirability of sub-dividing the high frequency amateur bands into phone and c.w. sections." An appended note by the Society's Secretary informed: "We feel that any such sub-division should be on a voluntary basis rather than being achieved by government regulations in each country."

forward in Amateur Radio. There are many practical problems which must first be solved, however, and we would be remiss if we did not mention them. Perhaps the principal difficulty is the differences in attitude shown by the amateurs of various countries toward the two modes of emission. For example, in many countries the interest seems to run about the same whether it is in the first or the second mode. In other countries such as those of Latin America, the interest is about 80 per cent phone. Then, there are technical aspects of the problem—propagation conditions and, to some extent, power permitted amateurs in each country.

Another difficulty is the fact that under international and regional treaty allocations, the available widths of amateur bands differ in various countries. This is especially true under Atlantic City as compared to the 7 Mc. band. Finally the successful working of any such agreement, voluntary or backed up by law, would require entire unanimity on the part of the AMATEURS CONVENTION and OBSERVATION of the AMATEURS CONVENTION to be had. One small group of amateurs failing to observe an otherwise-agreed scheme would disrupt the entire plan.

In a practical approach to this problem, we must revise our thinking that it is simply a matter of making up a chart and dividing the bands as between (1) phone and (2) c.w. Actually, as a purely technical matter arising from the great number of U.S. amateurs, there must be three classifications —

1—U.S. phone;
2—Non-U.S. phone;
3—C.W.

At the same meeting WIA discussed the matter of world-wide contests sponsored by individual member societies. It was noted there had been some difficulties resulting from failure to notify amateur societies of the world sufficiently far in

The various certificates mentioned in these notes last month are now completed and outstanding DX Contest Certificates for the 1946 and 1947 Contests will be the first to be issued. There are some 800 to be made out and signed so please hang in there a while longer. Due to postage difficulties certificates for each Division will be sent to the Divisional Council for issue to the winners.

TECHNICALLY in the know

TO-DAY more than ever before, it is essential to keep fully informed on electronic matters

RADIOTRON offers a technical service on valve applications that is unique in the radio world.

RADIOTRON TECHNICAL PUBLICATIONS INCLUDE

- I.** "Radiotronics" quarto size—20 pages per issue—sections devoted to DESIGN, THEORY, CIRCUITS and VALVE DATA—published every other month.
Handy filing covers are supplied with available back issues to "Radiotronics" subscribers.



- II.** Data Book—octavo size 150 sheets in loose leaf binder—comprehensive data on all Australian-made receiving types new and revised sheets released periodically.

- III.** Valve Charts—quarto size—36 pages covering characteristics, classification tables, socket connections—special section on Australian-made types—comprehensive substitution directory.



plus

first-hand knowledge on power valves and allied types, cathode ray tubes, the miniature range, circuits and associated components, as released. This information is just another service offered you by Radiotron.

keep posted

on the latest developments in electronic research. Arrange for Radiotron Technical publications to reach you regularly through the mail. Full particulars are available on enquiry.

AMALGAMATED WIRELESS VALVE CO. PTY. LTD.

SALES PROMOTION AND ADVERTISING

47 YORK STREET (BOX 2514, G.P.O.), SYDNEY, N.S.W.

31Y—A. P. Thornton, 28a Mand St., North
Belwyn.
EJM—M. D. Lodge, 8 Birdwood St., North Zastr.

MEMBERSHIP CHANGES

30X—J. W. Watson, 127 Dundas St., South
Preston
3PV—D. B. Shaw, 682 Glenhurst Rd., Glen-
hurst.
3OV—W. J. M. Bridge, 14a Criss St., Hampton

SVB—Mrs. C. M. Adams, 7 Wellman St., Box 100, Natick, Mass.

KEMP—Rev. M. C. Fay, 186 Chatsworth Rd.
Cooperstown.
481. W. W. Newman, Collinsville.

44F—A J Ford, 75 Station St., Broual
KACD—C A. Doddridge, Keynton, S. A.
ACZ—R I Scott, 82 Pilsford Rd., Prospect

WOLF - R. N. Lane, 3 Park Place, Redfern West
WOLF - P. B. Whitford, Kojanup Rd, Katanning

FEDERAL QSL BUREAU
RAY JONES, VK3RJ, MANAGER
DEMETER DR. DEMER, Wadsworth, Kohler, 943.

Itzenhagen-Nordsee, Kampaliedung Lund 17, Schleswig-Holstein, Brit.-Zone, Germany, in requesting confirmation of a report, states, "QHLs are the only

broader. I think we have to wait long time for exploration of our licences and would much desire to exchange magazines, stamps and friendly correspondence.

Advice from Belgium notifies the death, on 1st November, 1947, of Maurice Caron, 30 rue Thiers.

Biography: Maurice was a short-
wave listener of many years' experience and well-
known throughout the amateur world.

He is located at "Warmandyte," Karing Ave., Mirroon. He will operate under

NON-MEMBER PROPOSER

The C.A.V.—national society of the Czech American, wishes it to be known that a public letter

very soft on all the amateur bands using the call sign OK3AA. It is believed that the pirate station is located in Central Germany.

The QTH of the re-established Amateur Society in Hong Kong is H.A.R.T.S., P.O. Box 541, Hong Kong.

CHANGES TO CALL SIGNS, ETC

19178A, U.S. Army Radio Station, APO843, New York

WGVN is U.S. Army Radio Station, APO843,
New York.
104H, QSL via ARI (He is ex-HAHC/18 and

[illegible]

TRY

GLO-RAD

PERSONAL SERVICE

PERSONAL SERVICE

Individual attention given to design and manufacture of SPECIAL Units and Components for AMATEUR Use.

Write or Call—

GLORAD ENGINEERING SERVICES1864. $P_{11} = P_{12} = P_{21} = P_{22} = 0$ (C, B, line = B1)186A Riversdale Rd., (Cr. Robinson Rd.)
HAMMORBY VICTORIA

HAWTHORN ————— VICTORIA

Phone: Day—WA 3819. Night—WX 3440

ADRIAN in operation shortly) Extra Signal Squads, M.E.L.F.S.
1022 (QSL via R.S.G.B.)
STJLJ (now QRT) was actually in Eritrea and NOT in Ethiopia. He did not and will not QSL.

HEIO located a various towns in Lucretia, where a qth at 17.0 is the port of station of 104910, Ralph (now) Partridge 37, Zurich 8, Switzerland. He was using 104910 during the latter months of 1947.

For the Philadelphians—CRIFR, Regie Laitrain, Casella 27, Paris, 1948, 1949.

Vic Kellner (VRVGS) hopes to get active on 50 Mc from Canberra very shortly, and in removing qth from his home QTH in Sydney for the purpose.

ONHIC is on 3515 Kc, daily from 0600 to 0700 GMT undervoting to contact VKs and ZLs.

The following is an up-to-date list of licences:
1. FUL—VR2AD, 2.3M, 2.4M, 2.5M, 2.6M, 2.7M, 2.8M, 2.9M, 3.0M, 3.1M, 3.2M, 3.3M, 3.4M, 3.5M, 3.6M, 3.7M, 3.8M, 3.9M, 4.0M, 4.1M, 4.2M, 4.3M, 4.4M, 4.5M, 4.6M, 4.7M, 4.8M, 4.9M, 5.0M, 5.1M, 5.2M, 164.3M, 164.4M, 164.5M, 164.6M, 164.7M, 164.8M, 164.9M, 165.0M, 165.1M, 165.2M, 165.3M, 165.4M, 165.5M, 165.6M, 165.7M, 165.8M, 165.9M, 166.0M, 166.1M, 1

terminal. Byron uses a Kingsley Converter ahead of an ART and Claude a double conversion super LARK to a EUBBS to 10.7 Mc. then to 435 Mc. Claude is also building a 100 watt Transmitter to 50 Mc. using 850 as should be in the running when the wind comes good. Ye scrubs is getting excellent reception also from the local doctor's dia., myrrine machine also had a m/c away.

There is no doubt that fashion moves in circles. Heard 41Q from his new QTH busy working 3GN one yesterday night, and was amazed when Kevin mentioned he was using an 6466 in a Hartley oscillator with 6 watts and, believe it or not, LDDP modulation. ("Gremilin" please note what you misread!) However the quality was better than others heard on the band.

3XO has erected a three element beam for 50 Mc. and is building a transmitter and converter for that band. 31Q has a self-excited job on 40 Mc. and reckons to work at least into Maryborough.

3DP is busy with a new shock, and when every thing is fitted and J.M. gets his ATO-ARE combination going he will have an 4th. setup. 3AKP is at present bogged down with power leaks, tough Keith when you help make the juice that makes the QRM. However Maxwell is due for further QRM as two of the jobs are busy writing.

Apart from the beautiful dithery notes heard on 50 Mc. ye scrubs by some outstanding miracle worked LQ4DJN on 14 Mc. so after nearly 10 years trying has at last made W.A.C. incidentally LQ4DJN had I suppose what one might term a 1925 note. Well, katz that's all for now—see you next back up—Sunday, 7th March, 30 p.m. on 7050 Kc.

NORTH-WESTERN ZONE

Delegos, out from the N-W Zone met together at the N.W. Zone on 14th and settled our difficulties re transport, a 1 element antenna, between the widely separated ends of the large zone by dividing the Zone into two. The new "Far North Western Zone" is beyond a line from Pineroo to Nyah on "Lakes in Millers and Guyra, Reneg, Swan, Hill and Beazee are the main centres in the N-W Zone, not to mention Quambatook!

RTS has had an operation followed by a couple of weeks in hospital, but is now home and was last reported as had building a V.L.O. 3DA is working DX on c.w. like nobody's business. The rotary works OK. is busy with a new receiver and in trade to rubi of the modulator. SCE is at Portland with family enjoying a well earned holiday. SLA has moved to Quambatook for some months but has not got on the air from the new location as

far. 3HR is rebuilding. There was much Ham talk when 31L, 3HR and 3BK all got together unexpectedly in Goulburn P.O. recently. Clyde Case (3rd op. of 3CH) now has a ticket and his call sign is VE3ACE. Associates, Bud Page and Wal Ioveland are hard at it practicing the code. 3BAC (with KYL and three junior ops) is at Edithvale on holidays. is working on design of triple detection crystal-controlled single-sideband receiver. Attended the state and Maffra Conventions recently.

QUEENSLAND

Nominations of office-bearers for the ensuing 12 months formed the main item of business at the January general meeting of the Queensland Division. The President (4AW) occupied the chair, with Secretary (ART) and Treasurer (4DS) also on the official lists. Mr. P. Kelly (4KB) who has held the position of Federal Councillor for the past twelve months advised the meeting of the invalidity of the election of the Federal Delegate made at the previous meeting, a mistake due to the fact that no Federal Convention was at that time in the hands of this Division. Nominations were again called for and F. M. Nolan (4FX) and H. McGregor (4RU) were elected. A ballot will be taken to determine who represents this State at Melbourne at Easter.

The President then called for nominations for office-bearers and was speedily nominated for the next six years by 4KB, seconded 4FX. Vice-presidents, 4KB was nominated by 4FX and seconded 4RU. 4RU was nominated by 4KB and seconded 4HR. The retiring secretary 4RT had the pleasure of seeing 4XG nominated for his position by 4HR, seconded 4HR for Treasurer, the man nominated was 4RY who like 4XG, is a newcomer to the club. 4XG was elected.

It was decided to create another position in the QNL Department making separate jobs of unpaid and unpaid cards. Those nominated were 4EN and 4RD, while for Library Manager 4LY and 4WP were nominated. 4LY later declining because of election for another position—that of Publicity Country men who look forward to VE4WI broadcasts will be pleased to learn that 4FX was recommended for the job of Station Manager. As before, Country Representatives will be 4SN, and "A.R." Sub-Editor, 4RU. Another new face at the Council table will be 4PR, the new trade man, recently returned from Gasm. 4RT moved that a new post be created for an Associates' Member Representative and the following were nominated: 4KP, 4TB and Mr. K. Robinson. The attendance at the meeting was quite large, being

in the vicinity of thirty, and the new Council should be truly representative.

Around 11.30 a.m. were called for and 4KB moved that Convention Delegates' expenses should be paid on a per capita basis by all Divisions. To assist the Fund for British Appeal an isolated tract, presented by member Mr. F. Marralough, was raised and yielded £5/10/- toward the fund. Thanks, c.m.i.

As the business part outlined occupied a considerable amount of time, no lecture was presented, and the meeting closed with the usual rag-chew around the coffee urn.

SOUTH AUSTRALIA

The monthly general meeting was held on Tuesday, 10th February, and a capacity audience was present. The weather was hot and decidedly "stacy", which was an asset in one respect as the few members who stayed away on account of the heat did so a good turn, because I don't think we could have crammed another one into the hall. Mr. Roy Buckfield (3DA), assisted by Mr. Capel, lectured on "Some Aspects of P.M. as Applied to Amateur Radio." Fortunately for me the lecture consisted of a particularly interesting film on film, but a usual amount of blackboard explanation and therefore an attempt to rewrite the lecture is almost impossible under those conditions. Besides to say "Book" is our star turn with regard to lectures and has never failed to deliver the goods. A vote of thanks was proposed by Warwick Persons (3JFS) which was received with acclamation by all present.

Amongst the visitors were Messrs. Phillips, Lampe, Jackson (VADJN), Mayman, Powell, Uatrup, Bazel, Warren, Wood, King, Rodgers, Peters and Jameson. Valuing Hams included Graham Pitt (3GP), Harold Weber (3WV), Bill Barber (3DX), and last but not least our first V.L.O. member, Miss Andrews, whose arrival caused quite a ripple of excitement among the "woives" present.

The meeting was decidedly culminated by Ted Cawthron (53J) who rose during general business and had his customary "wings", and does a good job at this and will in time be the cause of several over Hams getting on their feet and having a say. This is a good thing and should be encouraged. Although not taking his "wings" from a humorous angle, "don't" be deceived, he knows more about radio, Amateur Radio in particular, than a good many, and nobody has done more for the up and coming Hams than he. Ever ready with advice, both theoretical and practical, he is a typical Ham and everyone will readily admit that his "wings" are

RED LINE EQUIPMENT FOR THE AMATEUR

Multi Impedance Modulation Transformers

Heavy Duty Power Supplies

Swinging and Smoothing Chokes

High Tension Plate Transformers

Low Tension Filament Supplies*

Class B Driver Transformers

Wide Range Audio Equipment

Frequency Dividing Networks

* Insulated up to 4000 volts if required.

Workshops:
2 Coates Lane,
Melbourne
Cen. 4773

Red Line Equipment Pty. Ltd.
Incorporating SWALES & SWANN

City Office:
157 Elizabeth St.
MU 6895

A.G. HEALING

LIMITED

MANUFACTURERS AND
DISTRIBUTORS FOR.....

Electrical and Testing Instruments for all purposes made to British Standard specifications. Each instrument is accurate, \pm or $-$, to ± 2 per cent., and parts are heavily plated to prevent corrosion even under tropical conditions. "Healing" Electrical Meters equal the best imported types and will give accurate service for long periods under the most exacting conditions.



No. 10A round production mounting Black Bakelite Case.

Type No. 30A 4" square semi-flush Black Bakelite Case.



No. 20A 2 1/2" round flush mounting Black Bakelite Case.

These, and all other Healing Radio Electrical Testing Units, are manufactured in our own factories and available from A. G. Healing Ltd.

OTHER INSTRUMENTS INCLUDE:

Oscillators — Multi-Testers — Signal Tracers, etc.



ALSO MANUFACTURERS AND DISTRIBUTORS FOR



Golden Voice RADIO

A. G. HEALING LTD., Melbourne, Sydney, Adelaide

WESTERN AUSTRALIAN DISTRIBUTOR: Clock's Household Utilities, 858 High Street, Perth
BRISBANE REPRESENTATIVE: H. K. Lane, Basement, A.M.P. Building, Queen Street, Brisbane.
TASMANIAN REPRESENTATIVE: C. J. Irvine, P.O. Box 575, Launceston.

R.L.F.F.

Page 26

SEE .

Lawrence & Hanson's



Widest Possible Range of
RADIO PARTS

For the
**AMATEUR
BROADCASTER**

Experienced "hams" and the new comer to the interesting field of radio and amateur broadcasting find that all Lawrence & Hanson Radio Parts represent good solid value in both

SERVICE AND DEPENDABILITY.

Moreover L. & H. cater specially for the enthusiast who finds difficulty in obtaining certain parts, thus amateurs are assured that wherever possible Lawrence & Hanson will provide the most complete range of radio parts for their every requirement.

Designed by radio specialists and made to precision perfection, these high grade components guarantee longer life and greater serviceability to your radio equipment.

TECHNICAL ADVICE GIVEN ON REQUEST.

Obtain Lists and Prices from your Radio house.

LAWRENCE & HANSON
ELECTRICAL PTY. LTD.

93 YORK STREET, SYDNEY
120 COLLINS STREET, HOBART
87 ELIZABETH STREET, BRISBANE


172 WILLIAM STREET, MELBOURNE
60 WAYMOUTH STREET, ADELAIDE
20 PATERSON STREET, LAUNCESTON

MICROPHONES	CONDENSERS
COILS	CHOKES
BATTERIES	CHASSIS
METERS	SPEAKERS
SWITCHES	RESISTORS
VALVES	LINERFILTERS
VIBRATORS	TRANSFORMERS

Etc., Etc.

Hobbyists Build these two Aegis Models

There's pleasure and profit in building popular Aegis kit assemblies for your friends! Much in demand is the well-known model KP4, illustrated at right. It's a compact, efficient 4-valve Battery operated Portable which, when finished, measures only 8" x 6½" x 7". Every feature is the best and the Kit is fully licensed by A.R.T.S. & P. Retail price in all capital cities £16/17/6 (including valves and batteries).

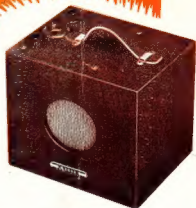

. . . and make your hobby PAY!



Attractive Nett Prices
For Trade
And Amateur.

First of a famous line of Aegis Kits is "The Little Companion" — a 5-valve 2-band receiver, A.C. operated. The Kit includes the handsome cabinet illustrated at left, which adds a final professional touch when you are assembling. See your nearest Aegis distributor for full details of those interesting offers.

AEGIS

MANUFACTURING COMPANY

Pty. Ltd.
208 L. LONSDALE ST., MELB.

:: THERE ARE AEGIS DISTRIBUTORS IN EVERY STATE ::